

Problem


2.1

See Excel Worksheet

Problem

2.2


Tap

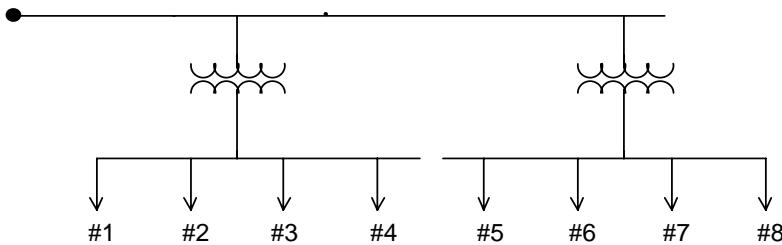

See Excel Worksheet.

Problem

2.3

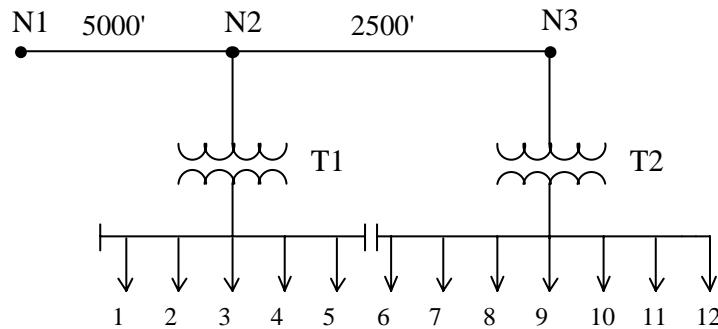

Problem 2.3.1-2.3.9

See Excel spreadsheet

Answers for 2.3.5, 2.3.6, and 2.3.9 are kW demands

Problem 2.3.j

$$V_{N1} := 2500 \cdot e^{j \cdot 0\text{deg}} \quad pf := .95 \quad kVA_{T1} := 25 \quad kVA_{T2} := 37.5 \quad kV_{hi} := 2.4 \quad V_{low} := 240$$

$$z_{line} := 0.306 + 0.6272j \quad zpu_{T1} := 0.018 \cdot e^{j \cdot 40\text{deg}} \quad zpu_{T2} := 0.02 \cdot e^{j \cdot 50\text{deg}}$$

$$D_{N1N2} := 5000 \quad D_{N2N3} := 2500$$

$$Z_{baseT1} := \frac{kV_{hi}^2 \cdot 1000}{kVA_{T1}} \quad Z_{baseT1} = 230.4000$$

$$Z_{T1} := zpu_{T1} \cdot Z_{baseT1} \quad Z_{T1} = 3.1769 + 2.6658j$$

$$Z_{\text{baseT2}} := \frac{kV_{\text{hi}}^2 \cdot 1000}{kVA_{\text{T2}}} \quad Z_{\text{baseT2}} = 153.6000$$

$$Z_{\text{T2}} := z_{\text{puT2}} \cdot Z_{\text{baseT2}} \quad Z_{\text{T2}} = 1.9746 + 2.3533j$$

$$z_{\text{N1N2}} := z_{\text{line}} \cdot \frac{D_{\text{N1N2}}}{5280} \quad z_{\text{N1N2}} = 0.2898 + 0.5939j$$

$$z_{\text{N2N3}} := z_{\text{line}} \cdot \frac{D_{\text{N2N3}}}{5280} \quad z_{\text{N2N3}} = 0.1449 + 0.2970j$$

Note: The voltage drops will be computed for a "worst case" situation. For each segment or transformer the maximum kVA demand on that segment or transformer will be used to compute the voltage drop to the remote end. This remote end voltage will then be assumed to be the voltage at that node when the maximum diversified demand downstream occurs.

$$kVADemand_{\text{N1}} := \frac{57.89}{\text{pf}} \cdot e^{j \cdot \text{acos(pf)}} \quad |kVADemand_{\text{N1}}| = 60.9368 \quad \frac{\arg(kVADemand_{\text{N1}})}{\deg} = 18.1949$$

$$I_{\text{N1N2}} := \frac{kVADemand_{\text{N1}}}{\frac{V_{\text{N1}}}{1000}} \quad |I_{\text{N1N2}}| = 24.3747 \quad \frac{\arg(I_{\text{N1N2}})}{\deg} = -18.1949$$

$$V_{\text{N2}} := V_{\text{N1}} - z_{\text{N1N2}} \cdot I_{\text{N1N2}} \quad |V_{\text{N2}}| = 2488.7963 \quad \frac{\arg(V_{\text{N2}})}{\deg} = -0.2658$$

$$kVADemand_{\text{T1}} := \frac{22.71}{\text{pf}} \cdot e^{j \cdot \text{acos(pf)}} \quad |kVADemand_{\text{T1}}| = 23.9053 \quad \frac{\arg(kVADemand_{\text{T1}})}{\deg} = 18.1949$$

$$I_{\text{T1}} := \frac{kVADemand_{\text{T1}}}{\frac{V_{\text{N2}}}{1000}} \quad |I_{\text{T1}}| = 9.6052 \quad \frac{\arg(I_{\text{T1}})}{\deg} = -17.9290$$

$$V_{\text{T1}} := V_{\text{N2}} - I_{\text{T1}} \cdot Z_{\text{T1}} \quad |V_{\text{T1}}| = 2451.9975 \quad \frac{\arg(V_{\text{T1}})}{\deg} = -0.6196$$

$$V_{\text{lowT1}} := V_{\text{T1}} \cdot \left(\frac{V_{\text{low}}}{kV_{\text{hi}} \cdot 1000} \right) \quad |V_{\text{lowT1}}| = 245.1998$$

$$kVADemand_{\text{N2}} := \frac{41.56}{\text{pf}} \cdot e^{j \cdot \text{acos(pf)}} \quad |kVADemand_{\text{N2}}| = 43.7474 \quad \frac{\arg(kVADemand_{\text{N2}})}{\deg} = 18.1949$$

$$I_{\text{N2N3}} := \frac{kVADemand_{\text{N2}}}{\frac{V_{\text{N1}}}{1000}} \quad |I_{\text{N2N3}}| = 17.4989 \quad \frac{\arg(I_{\text{N2N3}})}{\deg} = -18.1949$$

$$V_{N3} := V_{N2} - z_{N2N3} \cdot I_{N2N3} \quad |V_{N3}| = 2484.7879 \quad \frac{\arg(V_{N3})}{\deg} = -0.3619$$

$$V_{T2} := V_{N3} - I_{N2N3} \cdot Z_{T2} \quad |V_{T2}| = 2439.4506 \quad \frac{\arg(V_{T2})}{\deg} = -1.0341$$

$$V_{lowT2} := V_{T2} \cdot \left(\frac{V_{low}}{kV_{hi} \cdot 1000} \right) \quad |V_{lowT2}| = 243.9451$$

Problem

2.4

$$V_{N1} := 2500 \cdot e^{j \cdot 0 \deg} \quad pf := .95 \quad kVA_{T1} := 25 \quad kVA_{T2} := 37.5 \quad kV_{hi} := 2.4 \quad V_{low} := 240$$

$$Z_{line} := 0.306 + 0.6272j \quad zpu_{T1} := 0.018 \cdot e^{j \cdot 40 \deg} \quad zpu_{T2} := 0.02 \cdot e^{j \cdot 50 \deg}$$

$$D_{N1N2} := 5000 \quad D_{N2N3} := 2500$$

$$Z_{baseT1} := \frac{kV_{hi}^2 \cdot 1000}{kVA_{T1}} \quad Z_{baseT1} = 230.4000$$

$$Z_{T1} := zpu_{T1} \cdot Z_{baseT1} \quad Z_{T1} = 3.1769 + 2.6658j$$

$$Z_{baseT2} := \frac{kV_{hi}^2 \cdot 1000}{kVA_{T2}} \quad Z_{baseT2} = 153.6000$$

$$Z_{T2} := zpu_{T2} \cdot Z_{baseT2} \quad Z_{T2} = 1.9746 + 2.3533j$$

$$z_{N1N2} := z_{line} \cdot \frac{D_{N1N2}}{5280} \quad z_{N1N2} = 0.2898 + 0.5939j$$

$$z_{N2N3} := z_{line} \cdot \frac{D_{N2N3}}{5280} \quad z_{N2N3} = 0.1449 + 0.2970j$$

$$kWDemand_{N1} := 72.43 \quad pf := 0.95$$

$$kVA_{T1} := 25 \quad kVA_{T2} := 37.5$$

$$kVADemand_{N1} := \frac{kWDemand_{N1}}{pf} \cdot e^{j \cdot \arg(pf)} \quad |kVADemand_{N1}| = 76.2421 \quad \frac{\arg(kVADemand_{N1})}{\deg} = 18.1949$$

$$kVA_{total} := kVA_{T1} + kVA_{T2}$$

$$AF := \frac{kWDemand_{N1}}{kVA_{total}}$$

$$AF = 1.1589$$

$$kWDemand_{T1} := AF \cdot kVA_{T1} \quad kWDemand_{T1} = 28.9720$$

$$kWDemand_{T2} := AF \cdot kVA_{T2} \quad kWDemand_{T2} = 43.4580$$

$$kVADemand_{T1} := \frac{kWDemand_{T1}}{pf} \cdot e^{j \cdot (\cos(pf))}$$

$$|kVADemand_{T1}| = 30.4968$$

$$\frac{\arg(kVADemand_{T1})}{\deg} = 18.1949$$

$$kVADemand_{T2} := \frac{kWDemand_{T2}}{pf} \cdot e^{j \cdot (\cos(pf))}$$

$$|kVADemand_{T2}| = 45.7453$$

$$\frac{\arg(kVADemand_{T2})}{\deg} = 18.1949$$

Note: For all segment and transformer currents, for the constant current model the allocated kVA will be used along with the Node N1 voltage to compute the currents.

$$I_{N1N2} := \frac{kVADemand_{N1}}{\frac{V_{N1}}{1000}}$$

$$|I_{N1N2}| = 30.4968$$

$$\frac{\arg(I_{N1N2})}{\deg} = -18.1949$$

$$V_{N2} := V_{N1} - z_{N1N2} \cdot I_{N1N2}$$

$$|V_{N2}| = 2485.9908$$

$$\frac{\arg(V_{N2})}{\deg} = -0.3330$$

$$I_{T1} := \frac{kVADemand_{T1}}{\frac{V_{N1}}{1000}}$$

$$|I_{T1}| = 12.1987$$

$$\frac{\arg(I_{T1})}{\deg} = -18.1949$$

$$V_{T1} := V_{N2} - I_{T1} \cdot Z_{T1}$$

$$|V_{T1}| = 2439.2044$$

$$\frac{\arg(V_{T1})}{\deg} = -0.7808$$

$$V_{lowT1} := V_{T1} \cdot \left(\frac{V_{low}}{kV_{hi} \cdot 1000} \right)$$

$$|V_{lowT1}| = 243.9204$$

$$\frac{\arg(V_{lowT1})}{\deg} = -0.7808$$

$$kVADemand_{N2} := kVADemand_{T2}$$

$$|kVADemand_{N2}| = 45.7453$$

$$\frac{\arg(kVADemand_{N2})}{\deg} = 18.1949$$

$$I_{N2N3} := \frac{kVADemand_{N2}}{\frac{V_{N1}}{1000}}$$

$$|I_{N2N3}| = 18.2981$$

$$\frac{\arg(I_{N2N3})}{\deg} = -18.1949$$

$$V_{N3} := V_{N2} - z_{N2N3} \cdot I_{N2N3}$$

$$|V_{N3}| = 2481.8046$$

$$\frac{\arg(V_{N3})}{\deg} = -0.4336$$

$$V_{T2} := V_{N3} - I_{N2N3} \cdot Z_{T2}$$

$$|V_{T2}| = 2434.4435$$


$$\frac{\arg(V_{T2})}{\deg} = -1.1394$$

$$V_{lowT2} := V_{T2} \cdot \left(\frac{V_{low}}{kV_{hi} \cdot 1000} \right)$$

$$|V_{lowT2}| = 243.4443$$

Problem

2.5

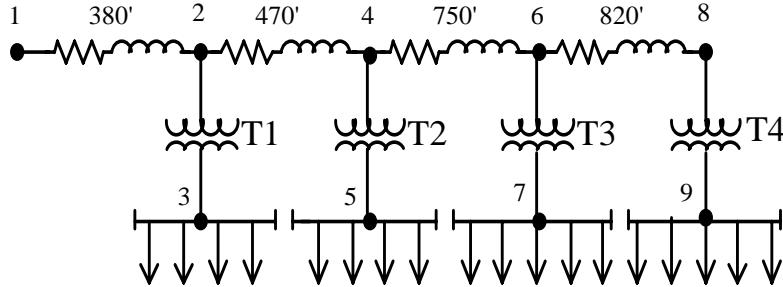

$$\text{CustMaxDem} := 15.5 + 7.5j$$

$$V_{N1} := 2600 \cdot e^{j \cdot 0^\circ}$$

$$\text{pf} := .95$$

$$Z_{line} := 0.4421 + 0.3213j$$

$$kVA_{T1} := 37.5$$

$$kVA_{T2} := kVA_{T1}$$

$$kVA_{T3} := 50$$

$$kVA_{T4} := kVA_{T3}$$

$$zpu_{T1} := 0.01 + 0.03j$$

$$zpu_{T2} := zpu_{T1}$$

$$zpu_{T3} := 0.015 + 0.035j$$

$$zpu_{T4} := zpu_{T3}$$

$$kV_{pu} := 2.4$$

$$V_{low} := 240$$

$$DF_4 := 2.1$$

$$DF_5 := 2.2$$

$$DF_{10} := 2.65$$

$$DF_{14} := 2.78$$

$$DF_{18} := 2.86$$

Problem 2.5.a

$$kVADemand_{T1} := \frac{4 \cdot \text{CustMaxDem}}{DF_4}$$

$$kVADemand_{T1} = 29.5238 + 14.2857j$$

$$kVADemand_{T2} := \frac{4 \cdot \text{CustMaxDem}}{DF_4}$$

$$kVADemand_{T2} = 29.5238 + 14.2857j$$

$$kVADemand_{T3} := \frac{5 \cdot \text{CustMaxDem}}{DF_5}$$

$$kVADemand_{T3} = 35.2273 + 17.0455j$$

$$kVADemand_{T4} := \frac{5 \cdot \text{CustMaxDem}}{DF_5}$$

$$kVADemand_{T4} = 35.2273 + 17.0455j$$

Problem 2.5.b

$$kVADemand_{N1N2} := \frac{18 \cdot \text{CustMaxDem}}{DF_{18}}$$

$$kVADemand_{N1N2} = 97.5524 + 47.2028j$$

$$kVADemand_{N2N4} := \frac{14 \cdot \text{CustMaxDem}}{DF_{14}}$$

$$kVADemand_{N2N4} = 78.0576 + 37.7698j$$

$$kVADemand_{N4N6} := \frac{10 \cdot \text{CustMaxDem}}{DF_{10}}$$

$$kVADemand_{N4N6} = 58.4906 + 28.3019j$$

$$kVADemand_{N6N8} := \frac{5 \cdot \text{CustMaxDem}}{DF_5}$$

$$kVADemand_{N6N8} = 35.2273 + 17.0455j$$

Problem 2.5.c

$$D_{N1N2} := 380$$

$$D_{N2N4} := 470$$

$$D_{N4N6} := 750$$

$$D_{N6N8} := 820$$

$$z_{N1N2} := z_{\text{line}} \cdot \frac{D_{N1N2}}{1000}$$

$$z_{N1N2} = 0.1680 + 0.1221j$$

$$z_{N2N4} := z_{\text{line}} \cdot \frac{D_{N2N4}}{1000}$$

$$z_{N2N4} = 0.2078 + 0.1510j$$

$$z_{N4N6} := z_{\text{line}} \cdot \frac{D_{N4N6}}{1000}$$

$$z_{N4N6} = 0.3316 + 0.2410j$$

$$z_{N6N8} := z_{\text{line}} \cdot \frac{D_{N6N8}}{1000}$$

$$z_{N6N8} = 0.3625 + 0.2635j$$

$$Z_{\text{baseT1}} := \frac{kV_{hi}^2 \cdot 1000}{kVA_{T1}}$$

$$Z_{\text{baseT1}} = 153.6000$$

$$Z_{\text{baseT3}} := \frac{kV_{hi}^2 \cdot 1000}{kVA_{T3}}$$

$$Z_{\text{baseT3}} = 115.2000$$

$$Z_{T1} := z_{pu_{T1}} \cdot Z_{\text{baseT1}}$$

$$Z_{T1} = 1.5360 + 4.6080j$$

$$Z_{T3} := z_{pu_{T3}} \cdot Z_{\text{baseT3}}$$

$$Z_{T3} = 1.7280 + 4.0320j$$

$$Z_{\text{baseT2}} := \frac{kV_{hi}^2 \cdot 1000}{kVA_{T2}}$$

$$Z_{\text{baseT2}} = 153.6000$$

$$Z_{\text{baseT4}} := \frac{kV_{hi}^2 \cdot 1000}{kVA_{T4}}$$

$$Z_{\text{baseT4}} = 115.2000$$

$$Z_{T2} := z_{pu_{T2}} \cdot Z_{\text{baseT2}}$$

$$Z_{T2} = 1.5360 + 4.6080j$$

$$Z_{T4} := z_{pu_{T4}} \cdot Z_{\text{baseT4}}$$

$$Z_{T4} = 1.7280 + 4.0320j$$

$$I_{N1N2} := \frac{kVADemand_{N1N2}}{\frac{V_{N1}}{1000}}$$

$$|I_{N1N2}| = 41.6817$$

$$\frac{\arg(I_{N1N2})}{\deg} = -25.8210$$

$$V_{N2} := V_{N1} - z_{N1N2} \cdot I_{N1N2}$$

$$|V_{N2}| = 2591.4805$$

$$\frac{\arg(V_{N2})}{\deg} = -0.0338$$

$$I_{T1} := \frac{kVADemand_{T1}}{\frac{V_{N2}}{1000}}$$

$$|I_{T1}| = 12.6563$$

$$\frac{\arg(I_{T1})}{\deg} = -25.7871$$

$$V_{T1} := V_{N2} - I_{T1} \cdot Z_{T1}$$

$$|V_{T1}| = 2549.0127$$

$$\frac{\arg(V_{T1})}{\deg} = -1.0247$$

$$V_{N3} := V_{T1} \cdot \left(\frac{V_{low}}{kV_{hi} \cdot 1000} \right)$$

$$|V_{N3}| = 254.9013$$

$$\frac{\arg(V_{N3})}{\deg} = -1.0247$$

$$I_{N2N4} := \frac{kVADemand_{N2N4}}{\frac{V_{N2}}{1000}}$$

$$|I_{N2N4}| = 33.4617$$

$$\frac{\arg(I_{N2N4})}{\deg} = -25.8548$$

$$V_{N4} := V_{N2} - z_{N2N4} \cdot I_{N2N4}$$

$$|V_{N4}| = 2583.0213$$

$$\frac{\arg(V_{N4})}{\deg} = -0.0676$$

$$I_{T2} := \frac{\overline{kVADemand_{T2}}}{\frac{V_{N4}}{1000}}$$

$$|I_{T2}| = 12.6977$$

$$\frac{\arg(I_{T2})}{\deg} = -25.7534$$

$$V_{T2} := V_{N4} - I_{T2} \cdot Z_{T2}$$

$$|V_{T2}| = 2540.4700$$

$$\frac{\arg(V_{T2})}{\deg} = -1.0662$$

$$V_{N5} := V_{T2} \cdot \left(\frac{V_{low}}{kV_{hi} \cdot 1000} \right)$$

$$|V_{N5}| = 254.0470$$

$$\frac{\arg(V_{N5})}{\deg} = -1.0662$$

$$I_{N4N6} := \frac{\overline{kVADemand_{N4N6}}}{\frac{V_{N4}}{1000}}$$

$$|I_{N4N6}| = 25.1558$$

$$\frac{\arg(I_{N4N6})}{\deg} = -25.8886$$

$$V_{N6} := V_{N4} - z_{N4N6} \cdot I_{N4N6}$$

$$|V_{N6}| = 2572.8734$$

$$\frac{\arg(V_{N6})}{\deg} = -0.1082$$

$$I_{T3} := \frac{\overline{kVADemand_{T3}}}{\frac{V_{N6}}{1000}}$$

$$|I_{T3}| = 15.2104$$

$$\frac{\arg(I_{T3})}{\deg} = -25.7128$$

$$V_{T3} := V_{N6} - I_{T3} \cdot Z_{T3}$$

$$|V_{T3}| = 2523.0500$$

$$\frac{\arg(V_{T3})}{\deg} = -1.1062$$

$$V_{N7} := V_{T3} \cdot \left(\frac{V_{low}}{kV_{hi} \cdot 1000} \right)$$

$$|V_{N7}| = 252.3050$$

$$\frac{\arg(V_{N7})}{\deg} = -1.1062$$

$$I_{N6N8} := \frac{\overline{kVADemand_{N6N8}}}{\frac{V_{N6}}{1000}}$$

$$|I_{N6N8}| = 15.2104$$

$$\frac{\arg(I_{N6N8})}{\deg} = -25.9292$$

$$V_{N8} := V_{N6} - z_{N6N8} \cdot I_{N6N8}$$

$$|V_{N8}| = 2566.1646$$

$$\frac{\arg(V_{N8})}{\deg} = -0.1351$$

$$I_{T4} := I_{N6N8}$$

$$|I_{T4}| = 15.2104$$

$$\frac{\arg(I_{T4})}{\deg} = -25.9292$$

$$V_{T4} := V_{N8} - I_{T4} \cdot Z_{T4}$$

$$|V_{T4}| = 2516.1944$$

$$\frac{\arg(V_{T4})}{\deg} = -1.1321$$

$$V_{N9} := V_{T4} \cdot \left(\frac{V_{low}}{kV_{hi} \cdot 1000} \right)$$

$$|V_{N9}| = 251.6194$$

$$\frac{\arg(V_{N9})}{\deg} = -1.1321$$

Definitions for Part 7

$$\begin{array}{llll} P_{3N2} := V_{N2} & P_{3N4} := V_{N4} & P_{3N6} := V_{N6} & P_{3N8} := V_{N8} \\ P_{3N3} := V_{N3} & P_{3N5} := V_{N5} & P_{3N7} := V_{N7} & P_{3N9} := V_{N9} \end{array}$$

Problem 2.5.d

$$kVADemand_{N1N2} = 97.5524 + 47.2028j$$

$$MaxDivDemand := \frac{kVADemand_{N1N2}}{18}$$

$$MaxDivDemand = 5.4196 + 2.6224j$$

$$kVADemand_{N2N4} := MaxDivDemand \cdot 14$$

$$kVADemand_{T1} := 4 \cdot MaxDivDemand$$

$$kVADemand_{N4N6} := MaxDivDemand \cdot 10$$

$$kVADemand_{T2} := 4 \cdot MaxDivDemand$$

$$kVADemand_{N6N8} := MaxDivDemand \cdot 5$$

$$kVADemand_{T3} := 5 \cdot MaxDivDemand$$

$$I_{N1N2} := \frac{\overline{kVADemand_{N1N2}}}{\frac{V_{N1}}{1000}}$$

$$|I_{N1N2}| = 41.6817 \quad \frac{\arg(I_{N1N2})}{\deg} = -25.8210$$

$$V_{N2} := V_{N1} - z_{N1N2} \cdot I_{N1N2}$$

$$|V_{N2}| = 2591.4805 \quad \frac{\arg(V_{N2})}{\deg} = -0.0338$$

$$I_{T1} := \frac{\overline{kVADemand_{T1}}}{\frac{V_{N2}}{1000}}$$

$$|I_{T1}| = 9.2931 \quad \frac{\arg(I_{T1})}{\deg} = -25.7871$$

$$V_{T1} := V_{N2} - I_{T1} \cdot Z_{T1}$$

$$|V_{T1}| = 2560.2226 \quad \frac{\arg(V_{T1})}{\deg} = -0.7582$$

$$V_{N3} := V_{T1} \cdot \left(\frac{V_{low}}{kV_{hi} \cdot 1000} \right)$$

$$|V_{N3}| = 256.0223 \quad \frac{\arg(V_{N3})}{\deg} = -0.7582$$

$$I_{N2N4} := \frac{\overline{kVADemand_{N2N4}}}{\frac{V_{N2}}{1000}}$$

$$|I_{N2N4}| = 32.5257 \quad \frac{\arg(I_{N2N4})}{\deg} = -25.8548$$

$$V_{N4} := V_{N2} - z_{N2N4} \cdot I_{N2N4}$$

$$|V_{N4}| = 2583.2579 \quad \frac{\arg(V_{N4})}{\deg} = -0.0666$$

$$I_{T2} := \frac{\overline{kVADemand_{T2}}}{\frac{V_{N4}}{1000}}$$

$$|I_{T2}| = 9.3226 \quad \frac{\arg(I_{T2})}{\deg} = -25.7544$$

$$V_{T2} := V_{N4} - I_{T2} \cdot Z_{T2}$$

$$|V_{T2}| = 2551.9395 \quad \frac{\arg(V_{T2})}{\deg} = -0.7965$$

$$V_{N5} := V_{T2} \cdot \left(\frac{V_{low}}{kV_{hi} \cdot 1000} \right)$$

$$|V_{N5}| = 255.1939$$

$$\frac{\arg(V_{N5})}{\deg} = -0.7965$$

$$I_{N4N6} := \frac{\overline{kVADemand_{N4N6}}}{\frac{V_{N4}}{1000}}$$

$$|I_{N4N6}| = 23.3066$$

$$\frac{\arg(I_{N4N6})}{\deg} = -25.8876$$

$$V_{N6} := V_{N4} - z_{N4N6} \cdot I_{N4N6}$$

$$|V_{N6}| = 2573.8559$$

$$\frac{\arg(V_{N6})}{\deg} = -0.1042$$

$$I_{T3} := \frac{\overline{kVADemand_{T3}}}{\frac{V_{N6}}{1000}}$$

$$|I_{T3}| = 11.6959$$

$$\frac{\arg(I_{T3})}{\deg} = -25.7168$$

$$V_{T3} := V_{N6} - I_{T3} \cdot Z_{T3}$$

$$|V_{T3}| = 2535.4711$$

$$\frac{\arg(V_{T3})}{\deg} = -0.8678$$

$$V_{N7} := V_{T3} \cdot \left(\frac{V_{low}}{kV_{hi} \cdot 1000} \right)$$

$$|V_{N7}| = 253.5471$$

$$\frac{\arg(V_{N7})}{\deg} = -0.8678$$

$$I_{N6N8} := \frac{\overline{kVADemand_{N6N8}}}{\frac{V_{N6}}{1000}}$$

$$|I_{N6N8}| = 11.6959$$

$$\frac{\arg(I_{N6N8})}{\deg} = -25.9252$$

$$V_{N8} := V_{N6} - z_{N6N8} \cdot I_{N6N8}$$

$$|V_{N8}| = 2568.6973$$

$$\frac{\arg(V_{N8})}{\deg} = -0.1249$$

$$I_{T4} := I_{N6N8}$$

$$|I_{T4}| = 11.6959$$

$$\frac{\arg(I_{T4})}{\deg} = -25.9252$$

$$V_{T4} := V_{N8} - I_{T4} \cdot Z_{T4}$$

$$|V_{T4}| = 2530.2006$$

$$\frac{\arg(V_{T4})}{\deg} = -0.8872$$

$$V_{N9} := V_{T4} \cdot \left(\frac{V_{low}}{kV_{hi} \cdot 1000} \right)$$

$$|V_{N9}| = 253.0201$$

$$\frac{\arg(V_{N9})}{\deg} = -0.8872$$

Definitions for Part 7

$$P4_{N2} := V_{N2} \quad P4_{N4} := V_{N4} \quad P4_{N6} := V_{N6} \quad P4_{N8} := V_{N8}$$

$$P4_{N3} := V_{N3} \quad P4_{N5} := V_{N5} \quad P4_{N7} := V_{N7} \quad P4_{N9} := V_{N9}$$

Problem 2.5.e

$$I_{Cust} := \frac{I_{N1N2}}{18}$$

$$I_{Cust} = 2.0845 - 1.0086j$$

$$I_{N2N4} := I_{Cust} \cdot 14$$

$$I_{N2N4} = 29.1824 - 14.1205j$$

$$I_{N4N6} := I_{Cust} \cdot 10$$

$$I_{N4N6} = 20.8445 - 10.0861j$$

$$I_{N6N8} := I_{Cust} \cdot 5$$

$$I_{N6N8} = 10.4223 - 5.0430j$$

$$I_{T1} := I_{Cust} \cdot 4$$

$$I_{T1} = 8.3378 - 4.0344j$$

$$I_{T2} := I_{Cust} \cdot 4$$

$$I_{T2} = 8.3378 - 4.0344j$$

$$I_{T3} := I_{Cust} \cdot 5$$

$$I_{T3} = 10.4223 - 5.0430j$$

$$I_{T4} := I_{Cust} \cdot 5$$

$$I_{T4} = 10.4223 - 5.0430j$$

$$V_{N2} := V_{N1} - z_{N1N2} \cdot I_{N1N2}$$

$$|V_{N2}| = 2591.4805$$

$$V_{T1} := V_{N2} - I_{T1} \cdot Z_{T1}$$

$$|V_{T1}| = \blacksquare$$

$$V_{N3} := V_{T1} \cdot \left(\frac{V_{low}}{kV_{hi} \cdot 1000} \right)$$

$$|V_{N3}| = 256.0305$$

$$V_{N4} := V_{N2} - z_{N2N4} \cdot I_{N2N4}$$

$$|V_{N4}| = 2583.2858$$

$$V_{T2} := V_{N4} - I_{T2} \cdot Z_{T2}$$

$$|V_{T2}| = 2552.1296$$

$$V_{N5} := V_{T2} \cdot \left(\frac{V_{low}}{kV_{hi} \cdot 1000} \right)$$

$$|V_{N5}| = 255.2130$$

$$V_{N6} := V_{N4} - z_{N4N6} \cdot I_{N4N6}$$

$$|V_{N6}| = 2573.9463$$

$$V_{T3} := V_{N6} - I_{T3} \cdot Z_{T3}$$

$$|V_{T3}| = 2535.8834$$

$$V_{N7} := V_{T3} \cdot \left(\frac{V_{low}}{kV_{hi} \cdot 1000} \right)$$

$$|V_{N7}| = 253.5883$$

$$V_{N8} := V_{N6} - z_{N6N8} \cdot I_{N6N8}$$

$$|V_{N8}| = 2568.8411$$

$$V_{T4} := V_{N8} - I_{T4} \cdot Z_{T4}$$

$$|V_{T4}| = 2530.7909$$

$$V_{N9} := V_{T4} \cdot \left(\frac{V_{low}}{kV_{hi} \cdot 1000} \right)$$

$$|V_{N9}| = 253.0791$$

$$\frac{\arg(V_{N2})}{\deg} = -0.0338$$

$$\frac{\arg(V_{T1})}{\deg} = -0.7554$$

$$\frac{\arg(V_{N3})}{\deg} = -0.7554$$

$$\frac{\arg(V_{N4})}{\deg} = -0.0666$$

$$\frac{\arg(V_{T2})}{\deg} = -0.7909$$

$$\frac{\arg(V_{N5})}{\deg} = -0.7909$$

$$\frac{\arg(V_{N6})}{\deg} = -0.1042$$

$$\frac{\arg(V_{T3})}{\deg} = -0.8584$$

$$\frac{\arg(V_{N7})}{\deg} = -0.8584$$

$$\frac{\arg(V_{N8})}{\deg} = -0.1249$$

$$\frac{\arg(V_{T4})}{\deg} = -0.8809$$

$$\frac{\arg(V_{N9})}{\deg} = -0.8809$$

Definitions for Part 7

$$P_{N2} := V_{N2} \quad P_{N4} := V_{N4} \quad P_{N6} := V_{N6} \quad P_{N8} := V_{N8}$$

$$P_{N3} := V_{N3} \quad P_{N5} := V_{N5} \quad P_{N7} := V_{N7} \quad P_{N9} := V_{N9}$$

Problem 2.5.f

$$\text{AF} := \frac{\text{kVADemand}_{N1N2}}{175} \quad \text{AF} = 0.5574 + 0.2697j$$

$$\text{kVADemand}_{T1} := \text{kVA}_{T1} \cdot \text{AF} \quad \text{kVADemand}_{T1} = 20.9041 + 10.1149j$$

$$\text{kVADemand}_{T2} := \text{kVA}_{T2} \cdot \text{AF} \quad \text{kVADemand}_{T2} = 20.9041 + 10.1149j$$

$$\text{kVADemand}_{T3} := \text{kVA}_{T3} \cdot \text{AF} \quad \text{kVADemand}_{T3} = 27.8721 + 13.4865j$$

$$\text{kVADemand}_{T4} := \text{kVA}_{T4} \cdot \text{AF} \quad \text{kVADemand}_{T4} = 27.8721 + 13.4865j$$

$$\text{kVADemand}_{N2N4} := \text{kVADemand}_{T2} + \text{kVADemand}_{T3} + \text{kVADemand}_{T4}$$

$$\text{kVADemand}_{N4N6} := \text{kVADemand}_{T3} + \text{kVADemand}_{T4}$$

$$\text{kVADemand}_{N6N8} := \text{kVADemand}_{T4}$$

$$I_{N1N2} := \frac{\overline{\text{kVADemand}_{N1N2}}}{\frac{V_{N1}}{1000}} \quad |I_{N1N2}| = 41.6817 \quad \frac{\arg(I_{N1N2})}{\deg} = -25.8210$$

$$V_{N2} := V_{N1} - z_{N1N2} I_{N1N2} \quad |V_{N2}| = 2591.4805 \quad \frac{\arg(V_{N2})}{\deg} = -0.0338$$

$$I_{T1} := \frac{\overline{\text{kVADemand}_{T1}}}{\frac{V_{N2}}{1000}} \quad |I_{T1}| = 8.9612 \quad \frac{\arg(I_{T1})}{\deg} = -25.7871$$

$$V_{T1} := V_{N2} - I_{T1} \cdot Z_{T1} \quad |V_{T1}| = 2561.3318 \quad \frac{\arg(V_{T1})}{\deg} = -0.7320$$

$$V_{N3} := V_{T1} \cdot \left(\frac{V_{\text{low}}}{kV_{\text{hi}} \cdot 1000} \right) \quad |V_{N3}| = 256.1332 \quad \frac{\arg(V_{N3})}{\deg} = -0.7320$$

$$I_{N2N4} := \frac{\overline{\text{kVADemand}_{N2N4}}}{\frac{V_{N2}}{1000}} \quad |I_{N2N4}| = 32.8576 \quad \frac{\arg(I_{N2N4})}{\deg} = -25.8548$$

$$V_{N4} := V_{N2} - z_{N2N4} I_{N2N4} \quad |V_{N4}| = 2583.1740 \quad \frac{\arg(V_{N4})}{\deg} = -0.0670$$

$$I_{T2} := \frac{\overline{kVADemand_{T2}}}{\frac{V_{N4}}{1000}}$$

$$V_{T2} := V_{N4} - I_{T2} \cdot Z_{T2}$$

$$V_{N5} := V_{T2} \cdot \left(\frac{V_{low}}{kV_{hi} \cdot 1000} \right)$$

$$I_{N4N6} := \frac{\overline{kVADemand_{N4N6}}}{\frac{V_{N4}}{1000}}$$

$$V_{N6} := V_{N4} - z_{N4N6} I_{N4N6}$$

$$I_{T3} := \frac{\overline{kVADemand_{T3}}}{\frac{V_{N6}}{1000}}$$

$$V_{T3} := V_{N6} - I_{T3} \cdot Z_{T3}$$

$$V_{N7} := V_{T3} \cdot \left(\frac{V_{low}}{kV_{hi} \cdot 1000} \right)$$

$$I_{N6N8} := \frac{\overline{kVADemand_{N6N8}}}{\frac{V_{N6}}{1000}}$$

$$V_{N8} := V_{N6} - z_{N6N8} I_{N6N8}$$

$$I_{T4} := I_{N6N8}$$

$$V_{T4} := V_{N8} - I_{T4} \cdot Z_{T4}$$

$$V_{N9} := V_{T4} \cdot \left(\frac{V_{low}}{kV_{hi} \cdot 1000} \right)$$

$$|I_{T2}| = 8.9900$$

$$|V_{T2}| = 2552.9663$$

$$|V_{N5}| = 255.2966$$

$$|I_{N4N6}| = 23.9733$$

$$|V_{N6}| = 2573.5031$$

$$|I_{T3}| = 12.0317$$

$$|V_{T3}| = 2534.0247$$

$$|V_{N7}| = 253.4025$$

$$|I_{N6N8}| = 12.0317$$

$$|V_{N8}| = 2568.1963$$

$$|I_{T4}| = 12.0317$$

$$|V_{T4}| = 2528.6015$$

$$|V_{N9}| = 252.8602$$

$$\frac{\arg(I_{T2})}{\deg} = -25.7540$$

$$\frac{\arg(V_{T2})}{\deg} = -0.7705$$

$$\frac{\arg(V_{N5})}{\deg} = -0.7705$$

$$\frac{\arg(I_{N4N6})}{\deg} = -25.8880$$

$$\frac{\arg(V_{N6})}{\deg} = -0.1057$$

$$\frac{\arg(I_{T3})}{\deg} = -25.7153$$

$$\frac{\arg(V_{T3})}{\deg} = -0.8916$$

$$\frac{\arg(V_{N7})}{\deg} = -0.8916$$

$$\frac{\arg(I_{N6N8})}{\deg} = -25.9266$$

$$\frac{\arg(V_{N8})}{\deg} = -0.1269$$

$$\frac{\arg(I_{T4})}{\deg} = -25.9266$$

$$\frac{\arg(V_{T4})}{\deg} = -0.9116$$

$$\frac{\arg(V_{N9})}{\deg} = -0.9116$$

Definitions for Part g

$$P6_{N2} := V_{N2} \quad P6_{N4} := V_{N4} \quad P6_{N6} := V_{N6} \quad P6_{N8} := V_{N8}$$

$$P6_{N3} := V_{N3} \quad P6_{N5} := V_{N5} \quad P6_{N7} := V_{N7} \quad P6_{N9} := V_{N9}$$

Problem 2.5.g

$$\%DiffN2_4 := \frac{|P4_{N2}| - |P3_{N2}|}{|P3_{N2}|} \cdot 100$$

$$\%DiffN3_4 := \frac{|P4_{N3}| - |P3_{N3}|}{|P3_{N3}|} \cdot 100$$

$$\%DiffN4_4 := \frac{|P4_{N4}| - |P3_{N4}|}{|P3_{N4}|} \cdot 100$$

$$\%DiffN5_4 := \frac{|P4_{N5}| - |P3_{N5}|}{|P3_{N5}|} \cdot 100$$

$$\%DiffN6_4 := \frac{|P4_{N6}| - |P3_{N6}|}{|P3_{N6}|} \cdot 100$$

$$\%DiffN7_4 := \frac{|P4_{N7}| - |P3_{N7}|}{|P3_{N7}|} \cdot 100$$

$$\%DiffN8_4 := \frac{|P4_{N8}| - |P3_{N8}|}{|P3_{N8}|} \cdot 100$$

$$\%DiffN9_4 := \frac{|P4_{N9}| - |P3_{N9}|}{|P3_{N9}|} \cdot 100$$

$$\%DiffN2_5 := \frac{|P5_{N2}| - |P3_{N2}|}{|P3_{N2}|} \cdot 100$$

$$\%DiffN3_5 := \frac{|P5_{N3}| - |P3_{N3}|}{|P3_{N3}|} \cdot 100$$

$$\%DiffN4_5 := \frac{|P5_{N4}| - |P3_{N4}|}{|P3_{N4}|} \cdot 100$$

$$\%DiffN5_5 := \frac{|P5_{N5}| - |P3_{N5}|}{|P3_{N5}|} \cdot 100$$

$$\%DiffN6_5 := \frac{|P5_{N6}| - |P3_{N6}|}{|P3_{N6}|} \cdot 100$$

$$\%DiffN7_5 := \frac{|P5_{N7}| - |P3_{N7}|}{|P3_{N7}|} \cdot 100$$

$$\%DiffN8_5 := \frac{|P5_{N8}| - |P3_{N8}|}{|P3_{N8}|} \cdot 100$$

$$\%DiffN9_5 := \frac{|P5_{N9}| - |P3_{N9}|}{|P3_{N9}|} \cdot 100$$

$$\%DiffN2_6 := \frac{|P6_{N2}| - |P3_{N2}|}{|P3_{N2}|} \cdot 100$$

$$\%DiffN3_6 := \frac{|P6_{N3}| - |P3_{N3}|}{|P3_{N3}|} \cdot 100$$

$$\%DiffN4_6 := \frac{|P6_{N4}| - |P3_{N4}|}{|P3_{N4}|} \cdot 100$$

$$\%DiffN5_6 := \frac{|P6_{N5}| - |P3_{N5}|}{|P3_{N5}|} \cdot 100$$

$$\%DiffN6_6 := \frac{|P6_{N6}| - |P3_{N6}|}{|P3_{N6}|} \cdot 100$$

$$\%DiffN7_6 := \frac{|P6_{N7}| - |P3_{N7}|}{|P3_{N7}|} \cdot 100$$

$$\%DiffN8_6 := \frac{|P6_{N8}| - |P3_{N8}|}{|P3_{N8}|} \cdot 100$$

$$\%DiffN9_6 := \frac{|P6_{N9}| - |P3_{N9}|}{|P3_{N9}|} \cdot 100$$

Node	Problem 4	Problem 5	Problem 6
2	$\%DiffN2_4 = 0.0000$	$\%DiffN2_5 = 0.0000$	$\%DiffN2_6 = 0.0000$
3	$\%DiffN3_4 = 0.4398$	$\%DiffN3_5 = 0.4430$	$\%DiffN3_6 = 0.4833$
4	$\%DiffN4_4 = 0.0092$	$\%DiffN4_5 = 0.0102$	$\%DiffN4_6 = 0.0059$
5	$\%DiffN5_4 = 0.4515$	$\%DiffN5_5 = 0.4590$	$\%DiffN5_6 = 0.4919$
6	$\%DiffN6_4 = 0.0382$	$\%DiffN6_5 = 0.0417$	$\%DiffN6_6 = 0.0245$

7	$\% \text{DiffN7}_4 = 0.4923$	$\% \text{DiffN7}_5 = 0.5086$	$\% \text{DiffN7}_6 = 0.4350$
8	$\% \text{DiffN8}_4 = 0.0987$	$\% \text{DiffN8}_5 = 0.1043$	$\% \text{DiffN8}_6 = 0.0792$
9	$\% \text{DiffN9}_4 = 0.5566$	$\% \text{DiffN9}_5 = 0.5801$	$\% \text{DiffN9}_6 = 0.4931$

Problem 2.1

1 For each of the customers determine:


- a. Maximum 15 minute kW demand
- b. Average 15 minute kW demand
- c. Total KWH usage in the 4 hour period
- d. Load factor

Customer	Customer	Customer	Customer
#1	#2	#3	#4
10.84	8.52	11.04	2.72
6.84	4.15	5.11	1.70
29.05	17.63	21.72	7.23
0.6306	0.4867	0.4629	0.6256

2. For the 25kVA transformer determine:

- a. Maximum 15 minute diversified demand **26.70**
- b. Maximum 15 minute non-coincident demand **33.12**
- c. Utilization Factor (assume unity power factor) **1.068**
- d. Diversity Factor **1.2404**
- e. Load Diversity **6.42**

3. Plot the "load duration curve" for the transformer

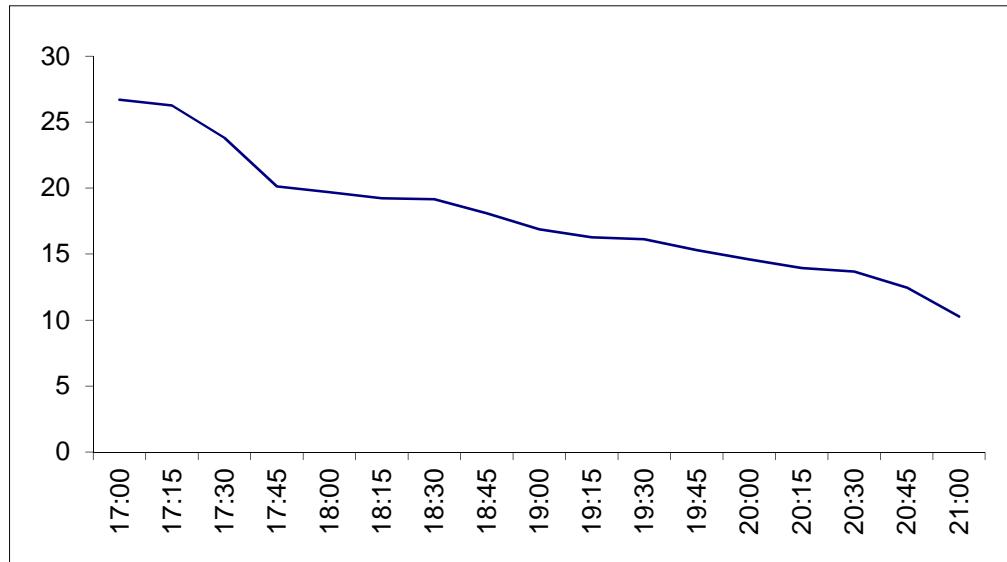

Problem 2.2

1 For each transformer determine:

	Trf #1	Trf #2
a. 30 minute maximum kVA demand	105	128
b. Non-coincident maximum kVA demand	130.00	170.00
c. Load factor	0.595238	0.686523
d. Diversity factor	1.2381	1.3281
e. Suggested transformer rating (50, 75, 100, 167)	75	100
f. Utilization factor	1.4	1.2800
g. Energy (kWh) during the 4 hour period	225	316.3500

2 Maximum diversified 30-minute kVA demand at the Tap **195**

Problem 2.3